 


# DIC HW2

312510190 張家瑋

## Exercise 2-1: 1-bit Full Adder standard cell



A	B	C	C <sub>out</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Implement 1-bit FA by XOR and MAJ gates in the cell library，實作結果如下:

```

41 x_xor1 a_in b_in      VDD GND ab_in XOR2x2_ASAP7_75t_R
42 x_xor2 ab_in c_in     VDD GND s_o  XOR2x2_ASAP7_75t_R
43 x_maj  a_in b_in c_in VDD GND c_o  MAJx2_ASAP7_75t_R
44

```

測出結果如下圖:

```

*****
.title ex2_1

***** transient analysis tnom= 25.000 temp= 25.000 *****
pwr= 5.3878u from= 0. to= 80.0000n
tphl_cout= 39.9992p targ= 2.0718n trig= 2.0318n
tr_sout= 43.9107p targ= 2.0757n trig= 2.0318n

***** job concluded
*****
.title ex2_1

***** job statistics summary tnom= 25.000 temp= 25.000 *****

```

power	Delay = tphl_cout
<b>5.3878 uW</b>	<b>39.9992 ps</b>

## Exercise 2-2: Different logic family of 1-bit Full Adders

CMOS:

```
*****
.title diff_logicfamily_1bit_fa

***** transient analysis tnom= 25.000 temp= 25.000 *****
average_power_cmos= 14.1882u from= 0. to= 640.0000n
average_power_cpl= 8.3654u from= 0. to= 640.0000n
average_power_dcvs= 5.1702u from= 0. to= 640.0000n
tphl_cout_cmos= 71.7991p targ= 5.2445n trig= 5.1727n
tr_sout_cmos= 49.7442p targ= 5.2224n trig= 5.1727n
tphl_cout_cpl= 187.4632p targ= 5.3601n trig= 5.1727n
tr_sout_cpl= 74.7973p targ= 5.2475n trig= 5.1727n
tphl_cout_dcvs= 841.1834p targ= 6.0138n trig= 5.1727n
tr_sout_dcvs= 2.0202n targ= 7.1929n trig= 5.1727n

***** job concluded
*****
.title diff_logicfamily_1bit_fa
```

```
***** Circuit Statistics *****
# nodes      =      29 # elements   =      58
# resistors  =       0 # capacitors =       2 # inductors   =       0
# mutual_inds =       0 # vccs      =       0 # vcvs       =       0
# cccs       =       0 # ccvs      =       0 # volt_srcs  =       4
# curr_srcs  =       0 # diodes    =       0 # bjts       =       0
# jfets      =       0 # mosfets   =      52 # U elements =       0
# T elements =       0 # W elements =       0 # B elements =       0
# S elements =       0 # P elements =       0 # va device  =       0
# vector_srcs =       0 # N elements =       0
```

CPL\_type:

```
*****
.title diff_logicfamily_1bit_fa

***** transient analysis tnom= 25.000 temp= 25.000 *****
average_power_cmos= 14.1882u from= 0. to= 640.0000n
average_power_cpl= 8.3654u from= 0. to= 640.0000n
average_power_dcvs= 5.1702u from= 0. to= 640.0000n
tphl_cout_cmos= 71.7991p targ= 5.2445n trig= 5.1727n
tr_sout_cmos= 49.7442p targ= 5.2224n trig= 5.1727n
tphl_cout_cpl= 187.4632p targ= 5.3601n trig= 5.1727n
tr_sout_cpl= 74.7973p targ= 5.2475n trig= 5.1727n
tphl_cout_dcvs= 841.1834p targ= 6.0138n trig= 5.1727n
tr_sout_dcvs= 2.0202n targ= 7.1929n trig= 5.1727n

***** job concluded
*****
.title diff_logicfamily_1bit_fa
```

```

# cccs      =      0 # ccvs      =      0 # volt_srcs =      4
# curr_srcs =      0 # diodes    =      0 # bjts      =      0
# jfets     =      0 # mosfets   =     44 # U elements =      0
# T elements =      0 # W elements =      0 # B elements =      0
# S elements =      0 # P elements =      0 # va device  =      0
# vector_srcs =      0 # N elements =      0

```

DCVS-type:

```

*****
.title diff_logicfamily_1bit_fa

***** transient analysis tnom= 25.000 temp= 25.000 *****
average_power_cmos= 14.1882u from= 0. to= 640.0000n
average_power_cpl= 8.3654u from= 0. to= 640.0000n
average_power_dcvs= 5.1702u from= 0. to= 640.0000n
tphl_cout_cmos= 71.7991p targ= 5.2445n trig= 5.1727n
tr_sout_cmos= 49.7442p targ= 5.2224n trig= 5.1727n
tphl_cout_cpl= 187.4632p targ= 5.3601n trig= 5.1727n
tr_sout_cpl= 74.7973p targ= 5.2475n trig= 5.1727n
tphl_cout_dcvs= 841.1834p targ= 6.0138n trig= 5.1727n
tr_sout_dcvs= 2.0202n targ= 7.1929n trig= 5.1727n

***** job concluded
*****
.title diff_logicfamily_1bit_fa

```

```

***** Circuit Statistics *****
# nodes      =      30 # elements =      56
# resistors   =      0 # capacitors =      2 # inductors =      0
# mutual_inds =      0 # vccs      =      0 # vcvs      =      0
# cccs        =      0 # ccvs      =      0 # volt_srcs =      4
# curr_srcs   =      0 # diodes    =      0 # bjts      =      0
# jfets       =      0 # mosfets   =     50 # U elements =      0
# T elements  =      0 # W elements =      0 # B elements =      0
# S elements  =      0 # P elements =      0 # va device  =      0
# vector_srcs =      0 # N elements =      0

```

	power	Performance (delay)	Area (transistor count)
CMOS	<b>14.1882 uW</b>	<b>74.7991 ps</b>	<b>52</b>
CPL-type	<b>8.3654 uW</b>	<b>187.4632 ps</b>	<b>44</b>
DCVS-type	<b>5.1702 uW</b>	<b>841.1834 ps</b>	<b>50</b>

## Exercise 2-3: Design a 4 - Bit Adder

Timing Report:

Point	Incr	Path
-----	-----	-----
input external delay	0.00	0.00 r
A[1] (in)	0.00	0.00 r
A2/A (Adder_1bit_2)	0.00	0.00 r
A2/U1/Y (INVx3_ASAP7_75t_R)	3.37	3.37 f
A2/U4/Y (NAND2x1p5_ASAP7_75t_R)	5.83	9.20 r
A2/U5/Y (NAND2xp5_ASAP7_75t_R)	8.25	17.45 f
A2/U10/Y (AND2x2_ASAP7_75t_R)	20.06	37.52 f
A2/U2/Y (NOR2x1p5_ASAP7_75t_R)	14.09	51.61 r
A2/Cout (Adder_1bit_2)	0.00	51.61 r
A3/Cin (Adder_1bit_1)	0.00	51.61 r
A3/U2/Y (NOR2x1p5_ASAP7_75t_R)	11.60	63.21 f
A3/U1/Y (NOR2x1p5_ASAP7_75t_R)	11.37	74.57 r
A3/Cout (Adder_1bit_1)	0.00	74.57 r
A4/Cin (Adder_1bit_0)	0.00	74.57 r
A4/U1/Y (NOR2xp67_ASAP7_75t_R)	8.99	83.57 f
A4/U3/Y (NOR2xp33_ASAP7_75t_R)	6.22	89.79 r
A4/Cout (Adder_1bit_0)	0.00	89.79 r
Output[4] (out)	0.00	89.79 r
data arrival time		89.79
max_delay	90.00	90.00
output external delay	0.00	90.00
data required time		90.00
-----	-----	-----
data required time		90.00
data arrival time		-89.79
-----	-----	-----
slack (MET)		0.21

1  
exit


Critical Path: A[0] 至 Output[4]

```


NAND2x1p5_ASAP7_75t_R U21 ( .A(A[0]), .B(B[0]), .Y(n15) );
NOR2xp33_ASAP7_75t_R U22 ( .A(n8), .B(n15), .Y(n16) );
NOR3xp33_ASAP7_75t_R U17 ( .A(n16), .B(n9), .C(n17), .Y(n10) );
NOR2xp67_ASAP7_75t_R U13 ( .A(n11), .B(n10), .Y(n21) );
MAJxp5_ASAP7_75t_R U25 ( .A(n21), .B(A[3]), .C(B[3]), .Y(n12) );
INVxp33_ASAP7_75t_R U26 ( .A(n12), .Y(Output[4]) );

```

Pattern:

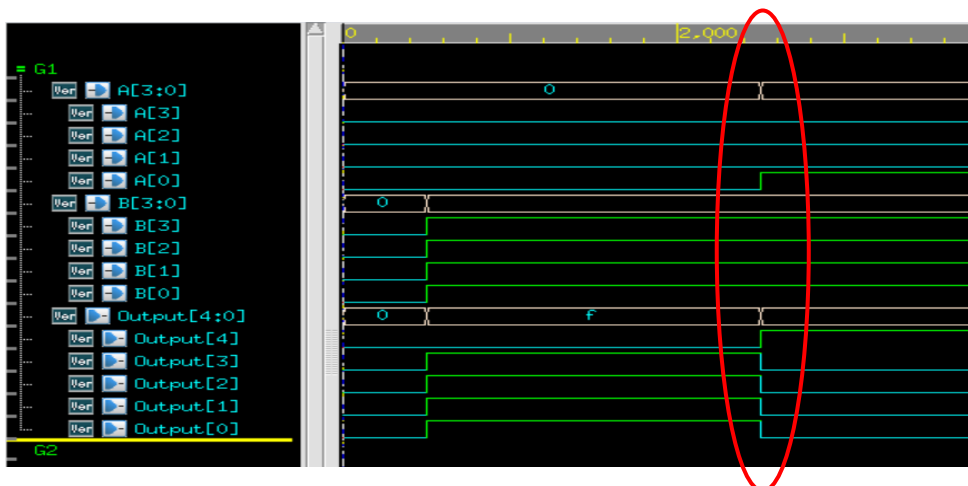
 
# Exercise 2-4: CMOS Logics for 4-Bit Adder



```
***** transient analysis tnom= 25.000 temp= 25.000 *****
avg_power_nand= 17.3089u from= 0. to= 6.0000n
worst_case_delay= 107.8989p targ= 3.1079n trig= 3.0000n
```

Power	17.3089 uW
worst delay	107.8989 ps

```
Radix 1 1 1 1 1 1 1 1
Vname A[3] A[2] A[1] A[0] B[3] B[2] B[1] B[0]
IO i i i i i i i i
Tunit ns
Period 0.2
Trise 0.00
Tfall 0.00
Tdelay 1
Vih 0.7
Vil 0.0
```

```
0 0 0 0 0 0 0 0
0 0 0 0 0 0 0 0
0 0 0 0 0 0 0 0
0 0 0 0 0 0 0 0
0 0 0 0 1 1 1 1
0 0 0 0 1 1 1 1
0 0 0 0 1 1 1 1
0 0 0 0 1 1 1 1
0 0 0 0 1 1 1 1
0 0 0 0 1 1 1 1
0 0 0 0 1 1 1 1
0 0 0 0 1 1 1 1
1 1 1 1 1 1 1 1
1 1 1 1 1 1 1 1
1 1 1 1 1 1 1 1
```

Worst delay case

Worst power case

由 2-2 的結果得知 Worst delay case 為 A[0]至 Output[4]；

當 B[3:0]為{1,1,1,1}時，假如 A[0]由 0 變為 1，Output[4]則會由 0 變為 1，此即為 Worst delay case